

19.1 Capacitors

Question Paper

Course	CIEA Level Physics
Section	19. Capacitance
Topic	19.1 Capacitors
Difficulty	Medium

Time allowed: 40

Score: /26

Percentage: /100

Question 1a

Define the capacitance of a parallel plate capacitor.

[2 marks]

Question 1b

Two capacitors, of capacitances, C_A and C_B , are connected in parallel to a power supply of electromotive force (e.m.f.) E , as shown in Fig. 1.1.

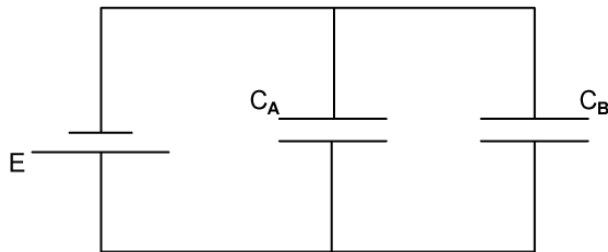


Fig. 1.1

Determine an expression for the combined capacitance C_C of the two capacitors.

[3 marks]

Question 1c

Two capacitors of capacitances $18\ \mu\text{F}$ and $51\ \mu\text{F}$, and resistor of resistance $4.5\ \text{k}\Omega$, are connected into the circuit of Fig. 1.2.

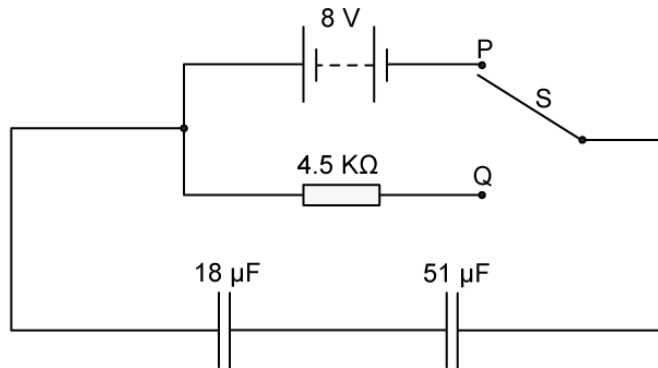


Fig. 1.2

The battery has an e.m.f of $8\ \text{V}$.

- (i)
Calculate the combined capacitance of the two capacitors.

[1]

- (ii)
The two-way switch S is initially at position P, so that the capacitors are fully charged.

Use the information in **(c) (i)** to calculate the total energy stored in the two capacitors.

total energy = J [2]

[3 marks]

Question 2a

Three capacitors, each of capacitance $27\ \mu\text{F}$, are connected as shown in Fig. 1.1.

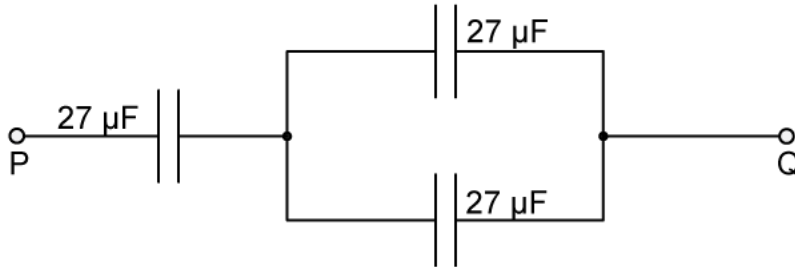


Fig. 1.1

Calculate the total capacitance between points P and Q.

capacitance = μF

[2 marks]

Question 2b

The maximum safe potential difference that can be applied across any one capacitor is $4\ \text{V}$.

Determine the maximum safe potential difference that can be applied between points P and Q.

potential difference = V

[2 marks]

Question 2c

A capacitor consists of an insulator separating two metal plates, as shown in Fig. 1.3.

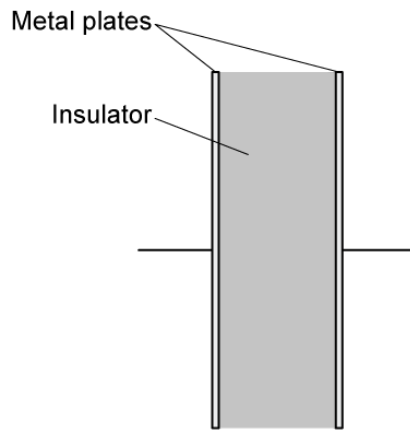


Fig. 1.3

The potential difference between the plates is V . The variation with V of the magnitude of the charge Q on one plate is shown in Fig. 1.4.

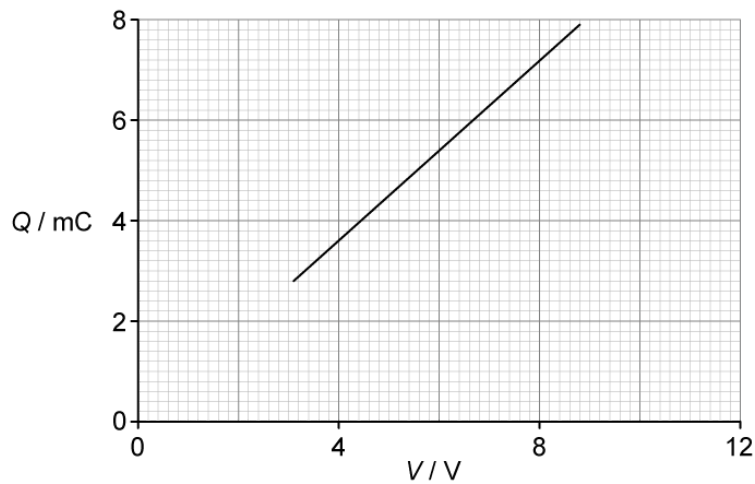


Fig1.4

Explain why the capacitor stores energy but not charge.

[3 marks]

Question 2d

Use Fig. 1.4 to determine:

- (i)
the capacitance of the capacitor

capacitance = μF [2]

- (ii)
the loss in energy stored in the capacitor when the potential difference V is reduced from 8 V to 6 V.

energy = mJ [2]

[4 marks]

Question 3a

State two functions of capacitors connected in electrical circuits.

[2 marks]

Question 3b

Three capacitors are connected in parallel to a power supply as shown in Fig. 1.1.

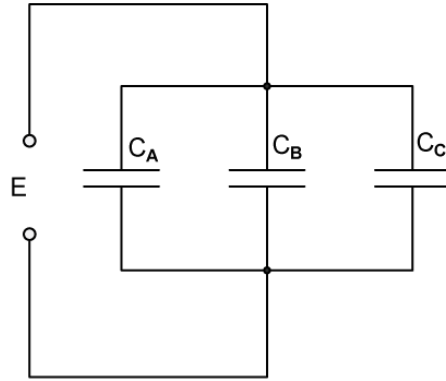


Fig. 1.1

The capacitors have a capacitance C_A , C_B and C_C . The power supply provides a potential difference E .

(i)

Explain why the charge on the positive plate of each capacitor is different.

[1]

(ii)

Use your answer in (i) to show that the combined capacitance C_T of the three capacitors is given by the expression.

$$C_T = C_A + C_B + C_C$$

[2]

[3 marks]

Question 3c

A student has available three capacitors, each of capacitance $24\ \mu\text{F}$.

Draw circuit diagrams, one in each case, to show how the student connects the three capacitors to provide a combined capacitance of:

(i)
 $36\ \mu\text{F}$

[1]

(ii)
 $16\ \mu\text{F}$

[1]

[2 marks]

Model Answers: Medium

1a

(a) The capacitance of a parallel plate capacitor is:

- Charge / potential difference; [1 mark]
- Where the charge is the charge on one plate, and the potential difference is across the two plates; [1 mark]

[Total: 2 marks]

1b

(b) Determine an expression for the combined capacitance C_C of the two capacitors:

Determine the p.d. across C_A and C_B :

- p.d. across both capacitors = E [1 mark]

Determine the total charge, Q_C in the circuit:

- $Q_C = Q_A + Q_B$ [1 mark]

Use the equation for p.d. and charge to determine an expression in terms of capacitance:

- $C = \frac{Q}{V}$ so $Q = VC$
- $EC_C = EC_A + EC_B$
- $C_C = C_A + C_B$ [1 mark]

[Total: 3 marks]

Remember that in a **parallel circuit**:

$$e.m.f. = p.d. 1 + p.d. 2....$$

$$Total\ charge = sum\ of\ charges\ across\ each\ branch$$

This is Kirchhoff's second law.

1c

(c)

List the known quantities:

- e.m.f., $E = 8 \text{ V}$
- $C_1 = 18 \mu\text{F} = 18 \times 10^{-6} \text{ F}$
- $C_2 = 51 \mu\text{F} = 51 \times 10^{-6} \text{ F}$

(i) Calculate the combined capacitance of the two capacitors:

Obtain an expression for the total capacitance of the two capacitors in a series circuit:

- $\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2}$
- $\frac{1}{18} + \frac{1}{51} = 0.075$
- $\frac{1}{0.075} = 13.3 \mu\text{F} = 13 \mu\text{F} \text{ (2 s.f.) [1 mark]}$

(ii) Calculate the total energy stored in the two capacitors:

- $\text{energy} = \frac{1}{2}CV^2 \text{ [1 mark]}$
- $\text{energy} = \frac{1}{2} \times (13 \times 10^{-6}) \times 8^2$
- $\text{energy} = 4.16 \times 10^{-4} \text{ J [1 mark]}$

[Total: 3 marks]

2a

(a) Calculate the total capacitance between points P and Q:

List the known quantities:

- Capacitance of each capacitor, $C = 27 \mu\text{F}$

Calculate the capacitance of the parallel combination, C_P :

- $C_P = C + C$
- $C_P = 27 + 27$
- $C_P = 54 \mu\text{F}$ [1 mark]

Calculate the capacitance of the series combination, C_S :

- $\frac{1}{C_S} = \frac{1}{C_P} + \frac{1}{C}$
- $\frac{1}{C_S} = \frac{1}{54} + \frac{1}{27} = \frac{1}{18}$
- $C_S = 18 \mu\text{F}$ [1 mark]

[Total: 2 marks]

You do not need to convert the capacitance from μF into F because the final answer is required in μF .

2b

(b) Determine the maximum safe potential difference that can be applied between points P and Q:

List the known quantities:

- Max p.d. across each capacitor = 4 V
- Capacitance of each capacitor, $C = 27 \times 10^{-6} \text{ F}$ (From part (a))
- Capacitance across the parallel combination, $C_P = 54 \times 10^{-6} \text{ F}$ (From part (a))

Calculate the safe p.d. across the parallel combination:

- For components in series, the charge across each component is the same
 - Consider the single capacitor as component 1 and the parallel combination as component 2 in the circuit
 - Hence, $Q_1 = Q_2$
- The total charge from P to Q = charge across the single capacitor
 - $Q_1 = C_1 V_{\text{max}}$
 - $Q_1 = (27 \times 10^{-6}) \times 4$
 - $Q_1 = 1.08 \times 10^{-4} \text{ C}$
- So, the p.d. across the parallel combination is:


$$\circ V_2 = \frac{Q_2}{C_p} = \frac{(1.08 \times 10^{-4})}{(54 \times 10^{-6})} = 2 \text{ V [1 mark]}$$

Calculate the p.d. across the series combination:

- p.d. in series combination = p.d. in parallel + p.d. across single
- p.d. in series combination = $2 + 4 = 6 \text{ V [1 mark]}$

[Total: 2 marks]

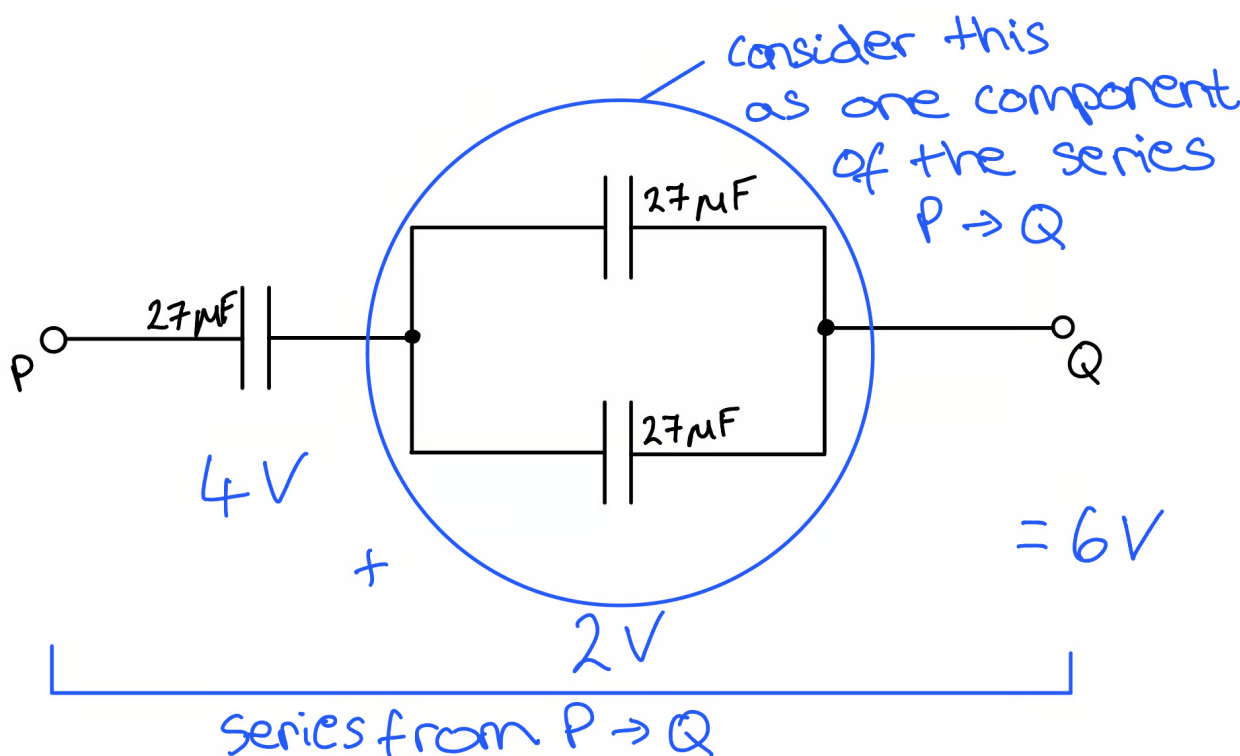If you're stuck on how the potential differences compare between the capacitors, this sketch might help:



2c

(c) The capacitor stores energy but not charge because:

- The charges on the plates of the capacitor are equal and opposite; [1 mark]
- So there is no resultant charge on the capacitor; [1 mark]
- But there is energy stored because there is a charge separation; [1 mark]

[Total: 3 marks]

2d

2d

(c) The capacitor stores energy but not charge because:

- The charges on the plates of the capacitor are equal and opposite; [1 mark]
- So there is no resultant charge on the capacitor; [1 mark]
- But there is energy stored because there is a charge separation; [1 mark]


[Total: 3 marks]

2d

(d)

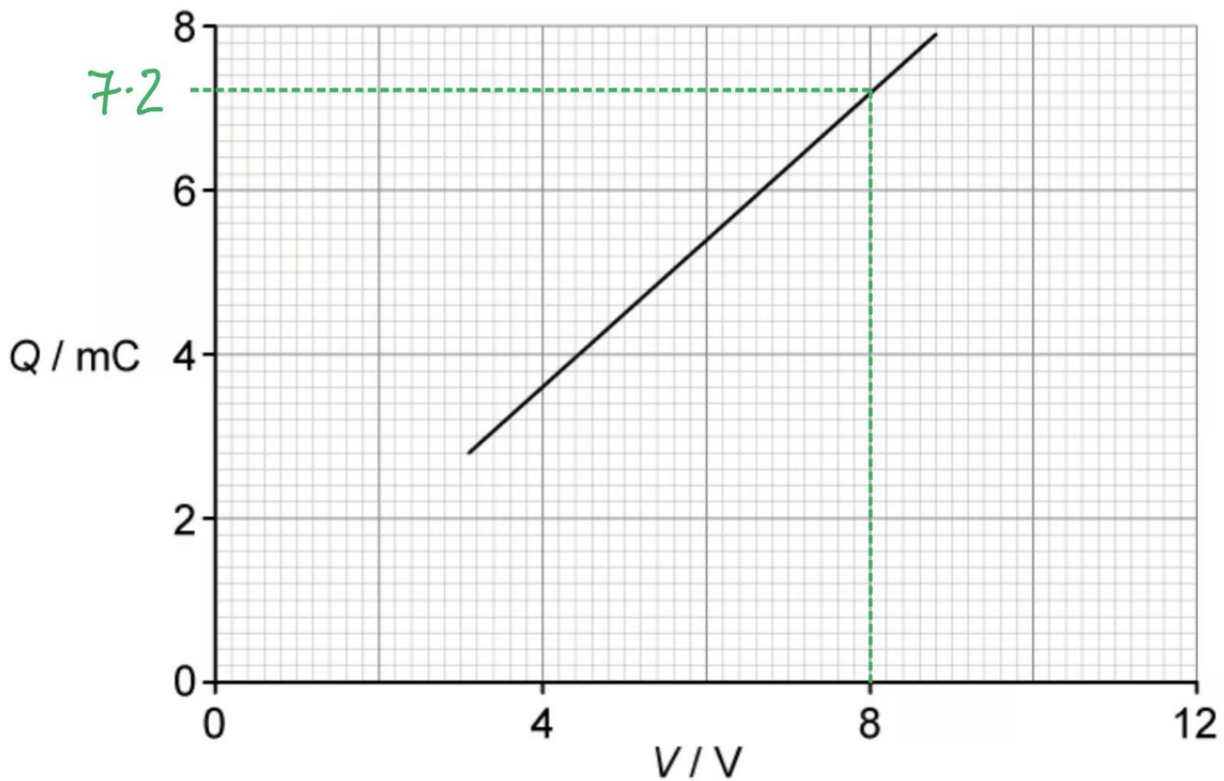(i) Determine the capacitance on the capacitor:

Draw lines on the graph to obtain a set of coordinates from the graph:



- p.d., $V = 8 \text{ V}$
- Charge, $Q = 7.2 \text{ mC}$


Calculate the capacitance:

- $C = \frac{Q}{V}$ [1 mark]

- $C = \frac{7.2 \times 10^{-3}}{8}$
- $C = 9 \times 10^{-4} \text{ F} = 900 \times 10^{-6} \mu\text{F}$ [1 mark]

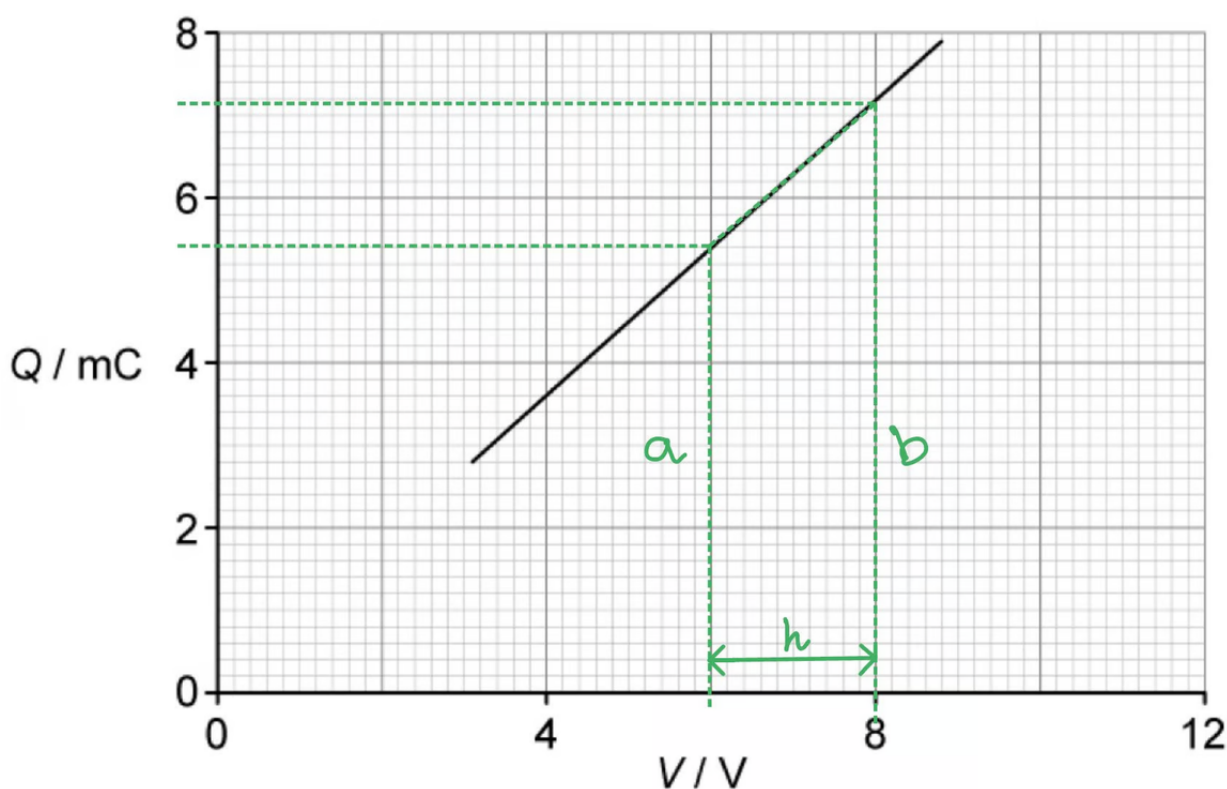(ii) Determine the loss in energy stored in the capacitor when the potential difference V is reduced from 8 V to 6 V:

Draw lines on the graph to identify the area of the trapezium underneath:



- $a = 5.4 \times 10^{-3} \text{ C}$
- $b = 7.2 \times 10^{-3} \text{ C}$
- $h = 2 \text{ V}$

Calculate the area of the trapezium under the graph:

- $A = \frac{1}{2}(a + b)h = \frac{1}{2}((5.4 \times 10^{-3}) + (7.2 \times 10^{-3})) \times 6$ [1 mark]
- $A = 0.0378 \text{ J} = 38 \text{ mJ}$ [1 mark]

[Total: 4 marks]

You will be expected to remember the equation for the area of a trapezium (and other

simple 2D shapes such as a right-angled triangle and rectangles) in your exam!

3a

(a) The functions of capacitors connected in electrical circuits are:

Any **two** from:

- To store energy; [1 mark]
- In smoothing circuits; [1 mark]
- To block direct current; [1 mark]
- In oscillators; [1 mark]

[Total: 2 marks]

To store **charge** is not an acceptable answer. Yes, a capacitor stores charge but it is not what it is used for in electrical circuits.

3b

(b)

(i) The charge on the positive plate of each capacitor is different because:

All **three** statements required for 1 mark:

- The potential difference across each capacitor is the same, E
- Each capacitor has a different capacitance
- $Q = CE$, so for each plate of the capacitor Q is different; [1 mark]

(ii) Show that the combined capacitance C_T of the three capacitors is given by the expression $C_T = C_A + C_B + C_C$:

Obtain an expression for the total charge across the capacitors in parallel:

- $Q_T = Q_A + Q_B + Q_C$ [1 mark]

Obtain an expression in terms of capacitance and p.d. for the total charge across the capacitors:

- $C_T E = C_A E + C_B E + C_C E$ [1 mark]
- Therefore, $C_T = C_A + C_B + C_C$

[Total: 3 marks]

The potential difference across each capacitor is the same **because** they are in parallel.

In part (ii), simplify the expression by **dividing** both sides **by E** to obtain the expression required.

3c

(c) Consider mathematically the combination of capacitors and their combined capacitance:

List the known quantities:

- Capacitance of each capacitor, $C = 24 \mu\text{F}$

Two capacitors in series with one in parallel:


- $C = \left(\frac{1}{\frac{1}{24} + \frac{1}{24}} \right) + 24 = 36 \mu\text{F}$
- Hence, this is the arrangement needed for (i)

Two capacitors in parallel with one in series:

- $C = \frac{1}{\left(\frac{1}{24 + 24} \right) + \frac{1}{24}} = 16 \mu\text{F}$
- Hence, this is the arrangement needed for (ii)


(i) A circuit diagram to show the 3 capacitors connected to obtain a capacitance of $36 \mu\text{F}$ is:

-

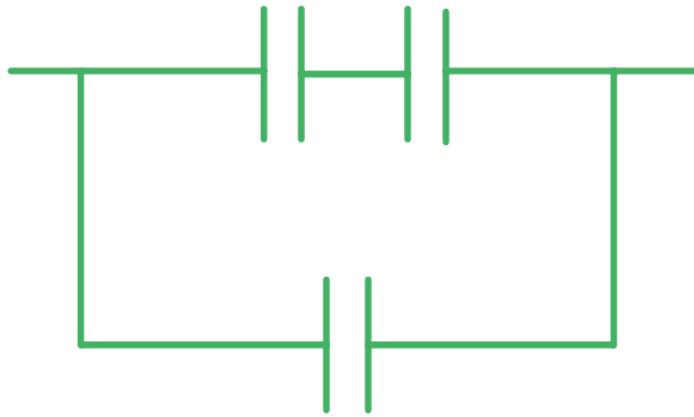

Two capacitors are drawn in series with one capacitor drawn in parallel to these;
[1 mark]

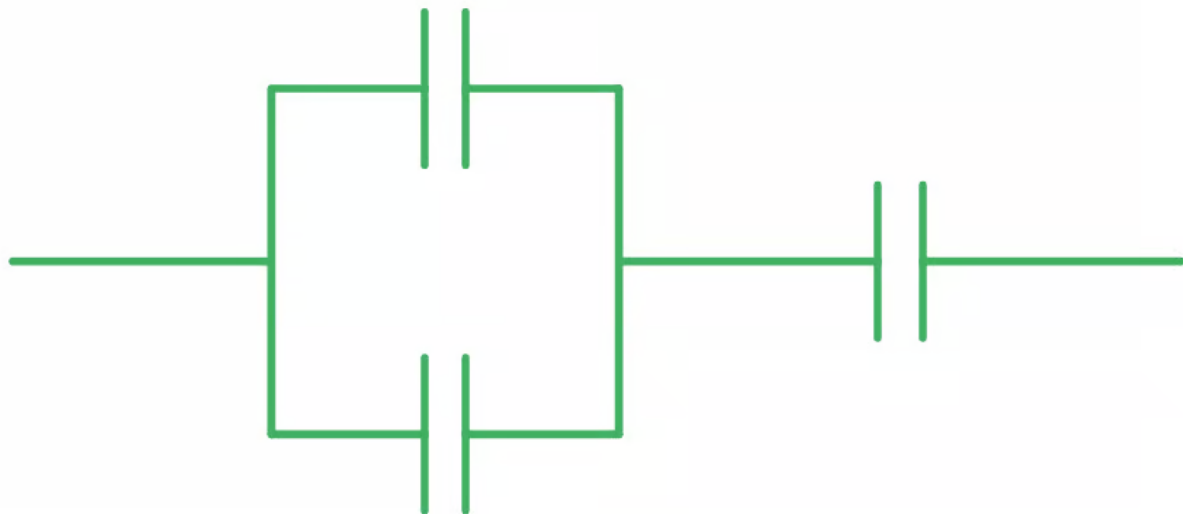(ii) A circuit diagram to show the 3 capacitors connected to obtain a capacitance of $16 \mu\text{F}$ is:



- Two capacitors are drawn in parallel with one capacitor in series to these; [1 mark]

[Total: 2 marks]

This question requires a bit of **trial and error** by considering the different combinations of capacitors in a logical order:

- All in parallel

- All in series
- Two in parallel and one in series – then mathematically you will notice this is an answer