

9.1 Current & Potential Difference

Question Paper

Course	CIEA Level Physics
Section	9. Electricity
Topic	9.1 Current & Potential Difference
Difficulty	Medium


Time allowed: 20

Score: /10

Percentage: /100

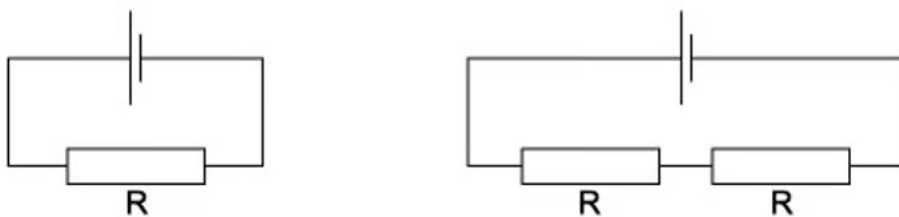Question 1

The diagrams show two different circuits.



The cells in each circuit have the same electromotive force and zero internal resistance. The three resistors each have the same resistance R .

In the circuit on the left, the power dissipated in the resistor is P .

What is the total power dissipated in the circuit on the right?

- A. $\frac{P}{4}$
- B. $\frac{P}{2}$
- C. P
- D. $2P$

[1 mark]

Question 2

The potential difference across a component in a circuit is 2.0 V.

How many electrons must flow through this component in order for it to be supplied with 4.8 J of energy?

- A. 2.6×10^{18}
- B. 1.5×10^{19}
- C. 3.0×10^{19}
- D. 6.0×10^{19}

[1 mark]

Question 3

Two lamps are connected in series to a 250V power supply. One lamp is rated 240V, 60W and the other is rated 10V, 2.5W.

Which statement most accurately describes what happens ?

- A. both lamps light at less than their normal brightness
- B. both lamps light normally
- C. only the 60 W lamp lights
- D. the 10 V lamp blows

[1 mark]

Question 4

Two copper wires of the same length but different diameters carry the same current.

Which statement about the flow of charged particles through the wires is correct?

- A. charged particles are provided by the power supply, therefore, the speed at which they travel depends only on the voltage of the supply
- B. the charged particles in both wires move with the same average speed because the current in both wires is the same
- C. the charged particles move faster through the wire with the larger diameter because there is a greater volume through which to flow
- D. the charged particles move faster through the wire with the smaller diameter because it has a larger potential difference applied to it

[1 mark]

Question 5

A power cable X has resistance R and carries current I .

A second cable Y has resistance $2R$ and carries current $\frac{I}{2}$

What is the ratio $\frac{\text{power dissipated in Y}}{\text{power dissipated in X}}$?

A. $\frac{1}{4}$

B. $\frac{1}{2}$

C. 2

D. 4

[1 mark]

Question 6

A milliammeter shows a reading of 20 mA.

How many electrons flow through the milliammeter in 10 seconds?

A. 0.20

B. 3.2×10^{20}

C. 200

D. 1.3×10^{18}

[1 mark]

Question 7

In a simple electrical circuit, the current in a resistor is measured as (2.50 ± 0.05) mA. The resistor is marked as having a value of $4.7\Omega \pm 2\%$.


If these values were used to calculate the power dissipated in the resistor, what would be the percentage uncertainty in the value obtained?

- A. 2 %
- B. 4 %
- C. 6 %
- D. 8 %

[1 mark]

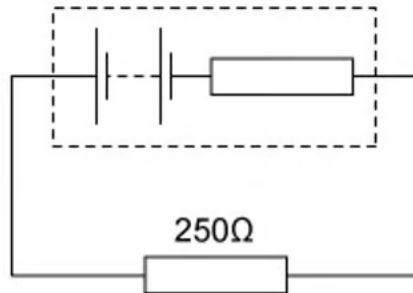Question 8

A battery, with a constant internal resistance, is connected to a resistor of resistance 250Ω , as shown.



The current in the resistor is 40 mA for a time of 60 s. During this time 6.0 J of energy is lost in the internal resistance.


What is the energy supplied to the external resistor during the 60 s and the e.m.f of the battery ?

	Energy / J	E. m. f / V
A	2.4	2.4
B	2.4	7.5
C	24	10.0
D	24	12.5

[1 mark]

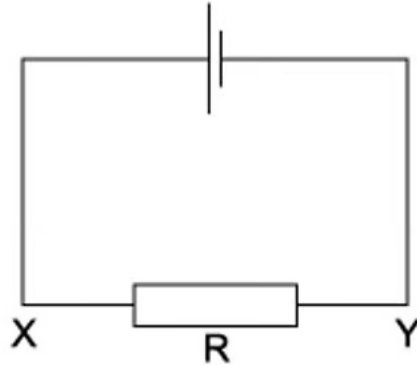Question 9

The current in the circuit shown is 4.8 A



What is the direction of flow and the rate of flow of electrons through the resistor R ?

	Direction of flow	Rate of flow
A	X to Y	$3.0 \times 10^{19} \text{ s}^{-1}$
B	X to Y	$6.0 \times 10^{18} \text{ s}^{-1}$
C	Y to X	$3.0 \times 10^{19} \text{ s}^{-1}$
D	Y to X	$6.0 \times 10^{18} \text{ s}^{-1}$

[1 mark]

Question 10

The charge that an electric battery can deliver is specified in ampere-hours.

For example, a battery of capacity 40 ampere-hours could supply, when fully charged, 0.2 A for 200 hours.

What is the maximum energy that a fully charged 12 V, 40 ampere-hour battery could supply?

- A. 1.7 kJ
- B. 29 kJ
- C. 1.7 MJ
- D. 29 MJ

[1 mark]

Model Answers: Medium

1

The correct answer is **B** because:

- Power is equal to $P = VI$
- Current is equal to $I = \frac{V}{R}$
- Combining the two equations gives
 - $P = V\left(\frac{V}{R}\right) = \frac{V^2}{R}$
- so, power dissipated in the circuit on the right is $P = \frac{V^2}{R}$
- The resistance in the circuit on the left is $2R$
- So, power dissipated in the circuit on the right is $\frac{V^2}{2R} = \frac{1}{2}\left(\frac{V^2}{R}\right) = \frac{P}{2}$
- Therefore, the power dissipated by the circuit on the right is $\frac{P}{2}$

2

The correct answer is **B** because:

- Potential difference is defined as the amount of electrical energy transferred between two points per unit of charge
 - In equation form this can be expressed as $V = \frac{E}{Q}$
 - Rearranging for charge Q gives $Q = \frac{E}{V}$
 - So, charge is equal to $Q = \frac{4.8}{2.0} = 2.4 \text{ C}$
- The total charge is equal to $Q = ne$
 - Where n is the number of electrons and e is the charge of one electron
- So, the number of electrons is equal to $n = \frac{Q}{e} = \frac{2.4}{1.6 \times 10^{-19}} = 1.5 \times 10^{19}$

3

The correct answer is **B** because:

- One lamp is rated 240 V, 60 W, this means that for the lamp to operate normally, there should be a potential difference (p.d.) of 240 V across it
- Electrical power is equal to $P = VI$
 - So, the current flowing through this lamp $= \frac{P}{V} = \frac{60}{240} = 0.25 \text{ A}$
- The other lamp is rated 10 V, 2.5 W. This lamp operates normally when there is a p.d. of 10 V across it
 - Current flowing through the lamp $= \frac{P}{V} = \frac{2.5}{10} = 0.25 \text{ A}$
- So, for normal operation, the same current of 0.25 A is required for both lamps. Since the lamps are connected in series, the same current would flow
 - So, both lamps light at their normal brightness
- In the same way, the sum of p.d. across the 2 lamps is equal to $240 + 10 = 250 \text{ V}$


4

The correct answer is **D** because:

- The equation for current in a current-carrying conductor is given by
 - $I = nAve$
 - Rearranging this for v we find $v = \frac{1}{nAe}$
- Since the current I , number of electrons n and charge e are the same for both wires, the electrons are faster in the thinner (smaller A) wire
 - In the next topic we will look more at resistivity in a wire, for now let's just consider the equation $R = \frac{\rho L}{A}$
- Since length L and resistivity ρ are the same for both wires, the thicker (larger A) wire will have a smaller resistance, so, the thinner wire will have a larger resistance
- Current is equal to $I = \frac{V}{R}$ for each wire, and since the wires have the same current I , the value of $\frac{V}{R}$ will be the same in each wire
- This means the thinner wire will have a larger resistance R and a smaller potential

difference V across it, while the thicker wire will have a smaller resistance R and a larger potential difference V across it

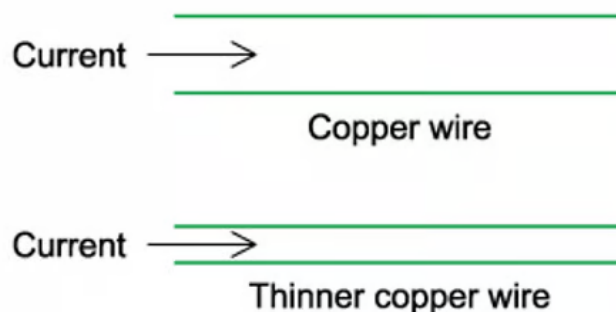- Therefore, the charged particles move faster through the thinner wire because it has a larger potential difference applied to it



A is incorrect because charged particles are not provided by the power supply, the charged particles (electrons) are already present in the copper wire

B is incorrect because the equation $\frac{1}{nAe}$ tells us the speed of the electrons depends on the thickness of the wire, so the speed will not be the same

C is incorrect because the equation $\frac{1}{nAe}$ tells us the electrons will be faster in the thinner wire (smaller A , larger v), not the thicker wire (larger A , smaller v)

5

The correct answer is **B** because:

- Power is equal to $P = VI$
- Potential difference is equal to $V = IR$
- Combining the two equations gives
 - $P = (IR)I = I^2R$
- The power dissipated in X is $= I^2R$
- The power dissipated in Y is $= \left(\frac{1}{2}\right)^2 (2R) = \frac{2I^2R}{4} = \frac{I^2R}{2}$
 - Therefore, the ratio $\frac{\text{power dissipated in Y}}{\text{power dissipated in X}} = \frac{I^2R}{2} \times \frac{1}{I^2R} = \frac{1}{2}$

6

The correct answer is **D** because:

- Charge is defined by $Q = I t$
- Current $I = 20 \times 10^{-3} \text{ A}$
- Time $t = 10 \text{ s}$
- So, charge $Q = (20 \times 10^{-3}) \times 10 = 0.2 \text{ C}$
- The total charge is equal to $Q = ne$
 - Where n is the number of electrons and e is the charge of one electron
- So, the number of electrons is equal to $n = \frac{Q}{e} = \frac{0.2}{1.6 \times 10^{-19}} = 1.25 \times 10^{18}$
 - Therefore, the number of electrons is 1.3×10^{18}

7

The correct answer is **C** because:

- Power is equal to $P = VI$
- Potential difference is equal to $V = IR$
- Combining the two equations gives
 - $P = (IR)I = I^2 R$
- First, we must convert the uncertainty in current to a percentage uncertainty so we can add the percentage uncertainties together
 - Current $I = 2.5 \text{ A}$
 - Uncertainty in current $\Delta I = 0.05 \text{ A}$
- So, the percentage uncertainty in current $= \frac{\Delta I}{I} \times 100 \% = \frac{0.05}{2.5} \times 100 = 2 \%$
- Since the power dissipated is given by $P = I^2 R$, the percentage uncertainty in power is $= (2 \times \% \text{ uncertainty in } I) + (\% \text{ uncertainty in } R)$
 - Therefore, $\% \text{ uncertainty in } P = (2 \times 2 \%) + 2\% = 4 + 2 = 6 \%$

8

The correct answer is **D** because:

- Power is equal to $P = VI = (IR)I = I^2 R$
- The energy transferred in external resistor is equal to $E = Pt = I^2 R t$

- Current $I = 20 \times 10^{-3} \text{ A}$
- Time $t = 10 \text{ s}$
- So, charge $Q = (20 \times 10^{-3}) \times 10 = 0.2 \text{ C}$
- The total charge is equal to $Q = ne$
 - Where n is the number of electrons and e is the charge of one electron
- So, the number of electrons is equal to $n = \frac{Q}{e} = \frac{0.2}{1.6 \times 10^{-19}} = 1.25 \times 10^{18}$
 - Therefore, the number of electrons is 1.3×10^{18}

7

The correct answer is **C** because:

- Power is equal to $P = VI$
- Potential difference is equal to $V = IR$
- Combining the two equations gives
 - $P = (IR)I = I^2 R$
- First, we must convert the uncertainty in current to a percentage uncertainty so we can add the percentage uncertainties together
 - Current $I = 2.5 \text{ A}$
 - Uncertainty in current $\Delta I = 0.05 \text{ A}$
- So, the percentage uncertainty in current $= \frac{\Delta I}{I} \times 100 \% = \frac{0.05}{2.5} \times 100 = 2 \%$
- Since the power dissipated is given by $P = I^2 R$, the percentage uncertainty in power is $= (2 \times \% \text{ uncertainty in } I) + (\% \text{ uncertainty in } R)$
 - Therefore, $\% \text{ uncertainty in } P = (2 \times 2 \%) + 2\% = 4 + 2 = 6 \%$

8

The correct answer is **D** because:

- Power is equal to $P = VI = (IR)I = I^2 R$
- The energy transferred in external resistor is equal to $E = Pt = I^2 R t$
 - Current $I = 40 \text{ mA} = 40 \times 10^{-3} \text{ A}$
 - Resistance $R = 250 \Omega$
 - Time $t = 60 \text{ s}$
- Energy transferred to the resistor $E = (40 \times 10^{-3})^2 \times 250 \times 60 = 24 \text{ J}$
 - Therefore, since 6 J of energy is lost in internal resistance, the battery must

supply a total of $6 + 24 = 30 \text{ J}$ of energy to the whole circuit

- The energy supplied by battery is $E = QV$
- Where Q is the charge and V is the e. m. f of the battery.
- Charge transferred, $Q = It = (40 \times 10^{-3}) \times 60 = 2.4 \text{ C}$
 - So, e. m. f of battery, $V = \frac{E}{Q} = \frac{30}{2.4} = 12.5 \text{ V}$

9

The correct answer is **C** because:

- Electrons flow from the negative terminal of the battery, since they are negatively-charged
- The negative terminal of the battery is represented by the shorter line at the symbol of the battery
 - So, the direction of flow of the electrons is from Y to X
- In terms of current, charge is defined as $Q = It$
- In terms of number of electrons, charge is equal to $Q = ne$
 - Where n and e are the number and charge of electrons respectively
- So, $ne = It$ and the rate of flow of electrons is equal to $\frac{n}{t} = \frac{1}{e}$
 - Rate of flow of electrons $= \frac{n}{t} = \frac{I}{e} = \frac{4.8}{1.6 \times 10^{-19}} = 3.0 \times 10^{19} \text{ s}^{-1}$

10

The correct answer is **C** because:

- Electrical power is equal to $P = VI$
- Power is also equal to $P = \frac{E}{t}$
 - Combining the two equations, $P = \frac{E}{t} = VI$
 - So, energy is equal to $E = VIt$
- The battery is described as '12 V, 40 ampere-hour', this means that the e. m. f. of the battery is $V = 12 \text{ V}$
- From the example given, 40 ampere-hours means that a current of 0.2 A can be supplied for 200 hours or $0.2 \text{ A} \times 200 \text{ h} = 40 \text{ Ah}$